

MG32F10x Application Note

1 ADC	3
-------------	---

1 ADC

When the ADC analog voltage input is $< 50\text{mV}$ while using MG32F103 and MG32F104 series, the sample circuit needs to be modified. The picture below is the reference design.

The sample circuit needs add R2 and R2 as below. The resistance of R1 can be modified, but the voltage of the voltage point in the picture must be $> 3.2\text{mV}$.

